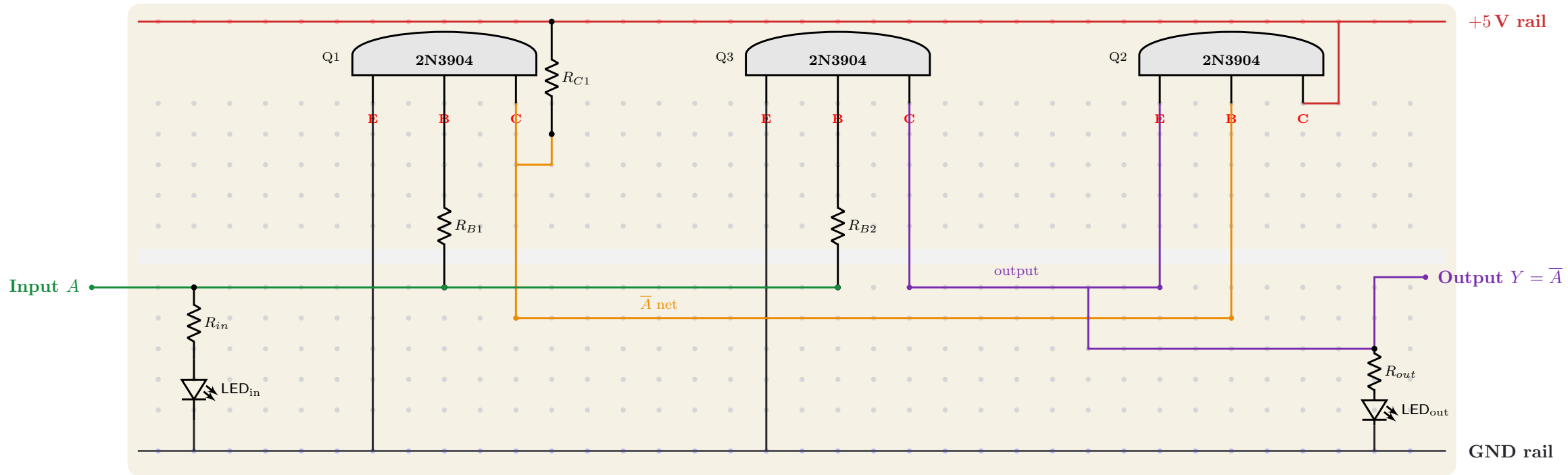




Jumper wires:

— +5 V — GND — input A — $\overline{A}$ — output

Each column of five holes in a bank is one node; transistor legs are E B C, left to right.