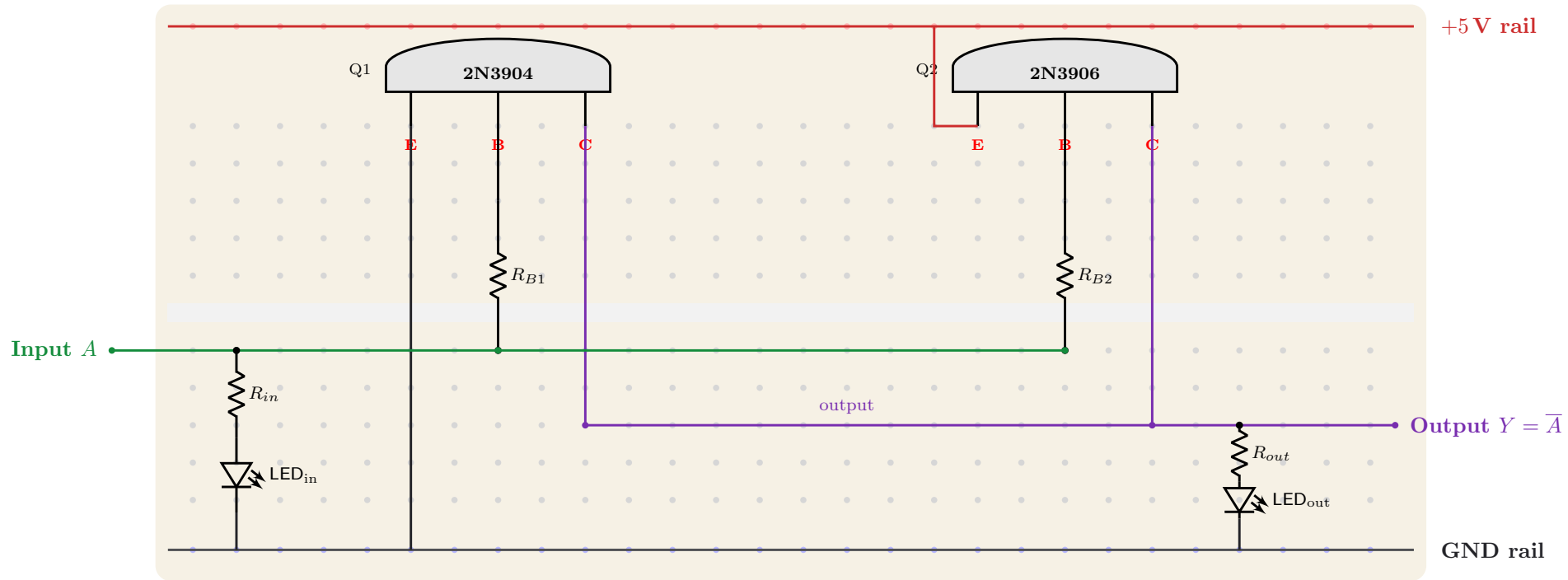




**Jumper wires:**

— +5 V    — GND    — input A    — output

*Each column of five holes in a bank is one node; transistor legs are E B C, left to right. Both parts share this pinout.*