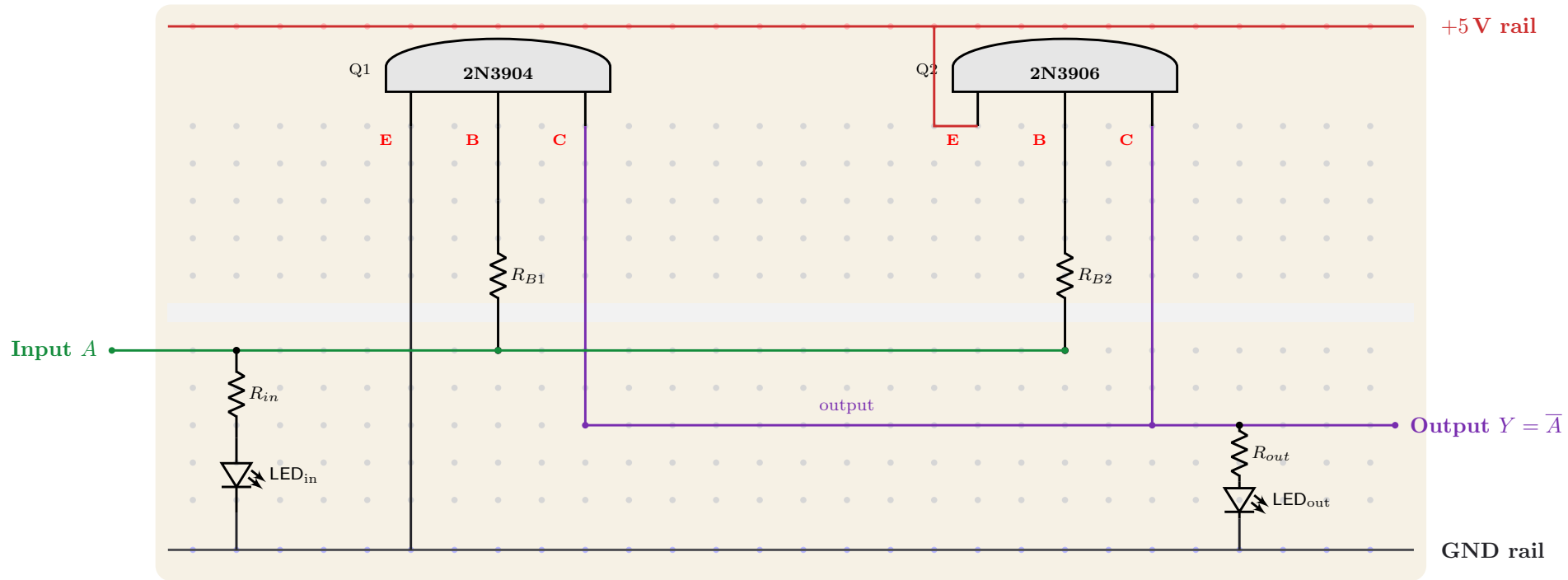




Jumper wires:

— +5 V — GND — input A — output

Each column of five holes in a bank is one node; transistor legs are E B C, left to right. Both parts share this pinout.